

Roll No. 3446065.....

3032

**B. Tech 3rd Semester (CSE)
Examination – December, 2019**

DIGITAL ELECTRONICS

Paper : PCC-CSE-205-G

Time : Three Hours]

[Maximum Marks : 75

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Attempt *five* questions in all, selecting *one* question from each Unit. Question Number 1 is *compulsory*. All questions carry equal marks.

1. (a) State the DE Morgan's Theorem. 2.5
- (b) What are the advantages and disadvantages of K-Method ? 2.5
- (c) What is Full adder ? 2.5
- (d) What is the difference between combinational circuits and sequential circuits ? 2.5

- (e) Explain D-type flip-flop. 2.5
- (f) Define Hold Time. 2.5

UNIT – I

2. (a) Realize AND, OR and NOT gate with the help of Universal gates NAND and NOR separately. 9
- (b) Implement Boolean expressions for EX-OR gate using NAND gates. 6
3. Write short notes on :
- (i) Error detecting and correcting code 8
- (ii) Excess-3 and gray code 7

UNIT – II

4. Realize a function with the help of NAND gates : 15
- $$F(A, B, C, D) = \Sigma(0, 1, 4, 6, 9, 12, 15) + d(2, 3, 6)$$
5. Write short notes on : 15
- (i) BCD adder circuit
- (ii) Priority Encoders
- (iii) Multiplexer

UNIT – III

6. (a) Explain the working of Master-Slave JK Flip flop. 9
- (b) What is the difference between Synchronous and Asynchronous counters ? 6

7. (a) Convert SR flip-flop to JK flip-flop. 9
(b) Explain the concept of Parallel to serial convertor. 6

UNIT – IV

8. (a) Implement a Full adder Using PLA. 9
(b) Explain the concept of Quantization and Encoding. 6
9. Write short note on : 15
- (i) Field Programmable Gate array
 - (ii) Complex programmable logic devices
 - (iii) Content Addressable Memory
-