

College Name :

DELHI GLOBAL INSTITUTE OF TECHNOLOGY

Name : BAZGHA RAZI







Course Code : PCC-CSE-205G

Subject : Digital Electronics

Session : 2019-2023

Ans 1a) ~~And~~ NAND and NOR are called universal gates. Because by using these gates we can implement any other gates.

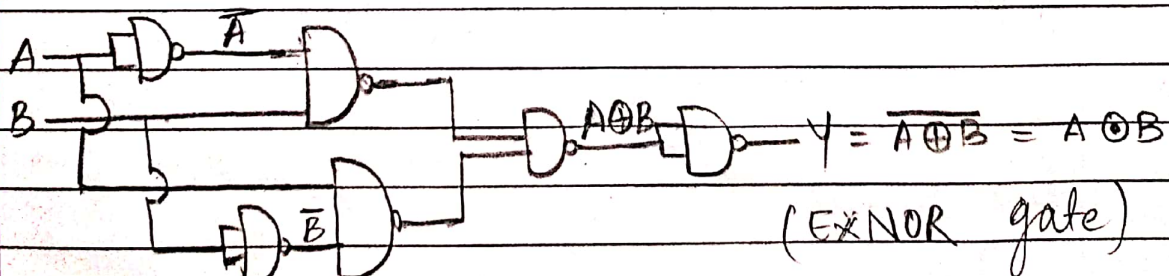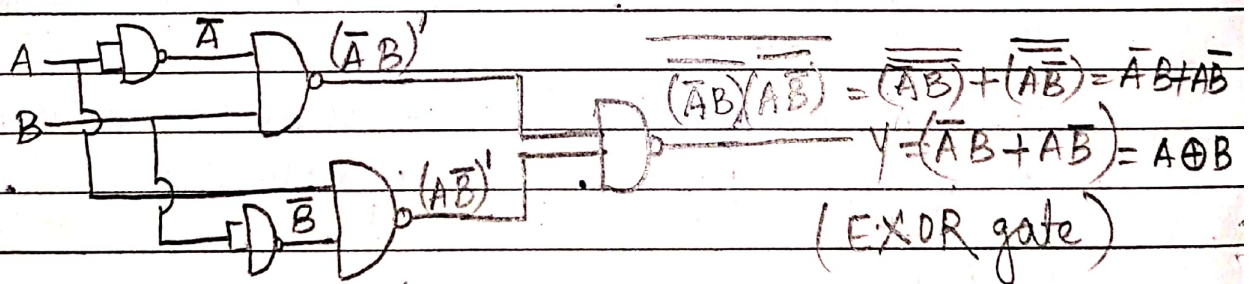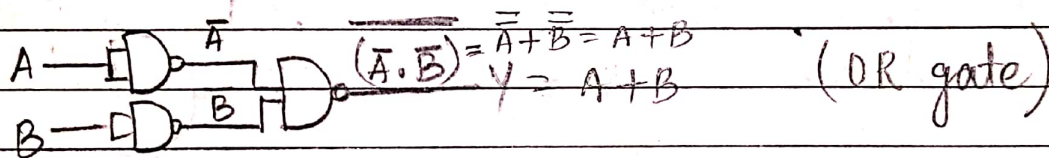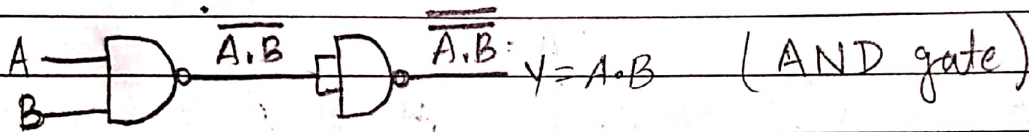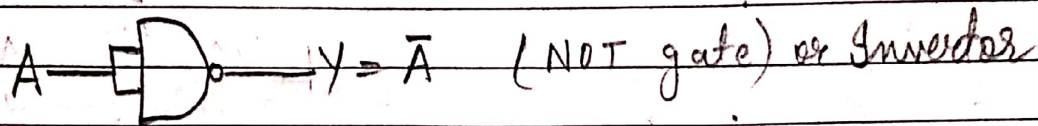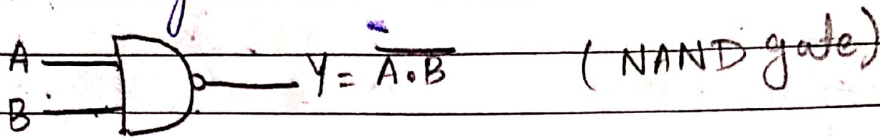For example by using NAND gate we make various gates:




ExNOR gate is the complemented form of EXOR gate.




# Using NOR gate


Page No.			
Date			

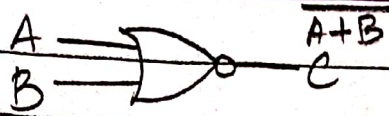


NOR gate

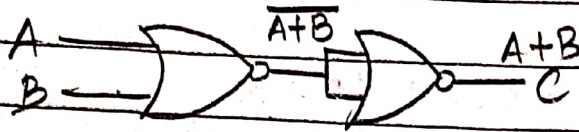


OR gate

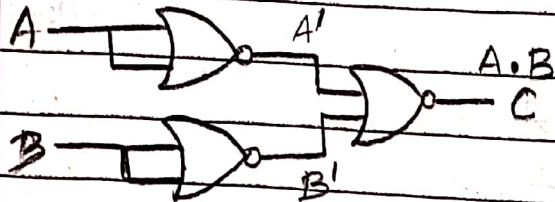


AND gate

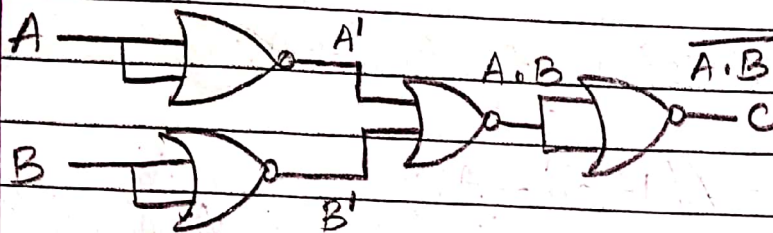


NAND gate

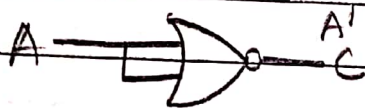


NOT gate (Inverter)

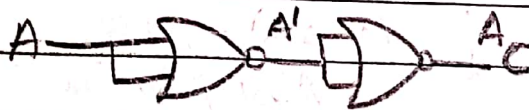

Buffer

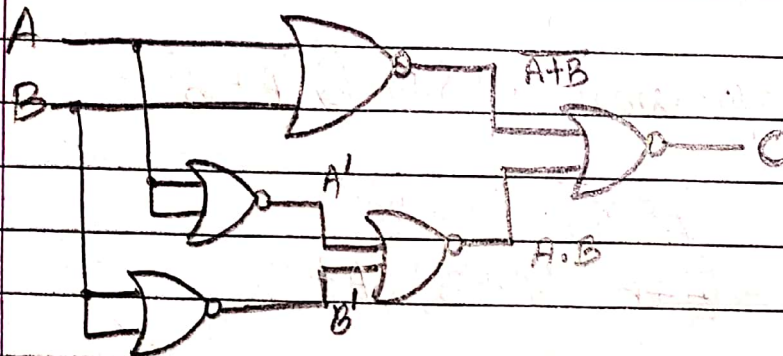

Exclusive - OR gate

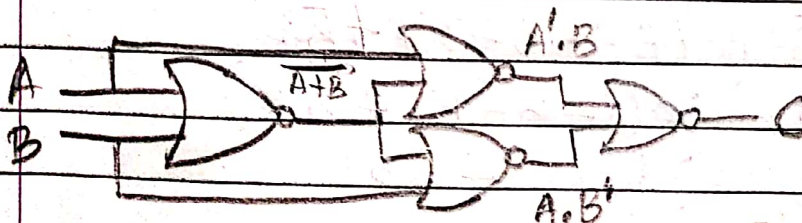

Exclusive - NOR gate



## Ans 1b) Combinational Circuits

## Sequential Circuits

- |   |  |
|---|--|
| <p>① It is the circuits whose output is determined by the present values of its input only.</p> <p>② It does not have a feedback path from output to input.</p> <p>③ It does not have a clock signal. Its action does not depend on clock transition.</p> <p>④ Its circuit is simpler than that of sequential logic circuits.</p> <p>⑤ It is built using basic gates i.e., NOT, AND, OR.</p> <p>⑥ Example: Adder, subtractor, multiplexer, etc.</p> | <p>① It is the circuits whose output is determined by the present values of the input as well as past values of the output.</p> <p>② It has a memory and a feedback path from output to input.</p> <p>③ It may or may not have clock signal but most sequential circuit have a clock signal.</p> <p>④ Its circuit is more complex than that of combinational circuits.</p> <p>⑤ It is built using basic gates and combinational circuits.</p> <p>⑥ Example: Flip-flops, counters, Shift registers.</p> |
|---|--|



## Ans 2a) De Morgan's Theorem

It works on the principle of duality.

Duality states that interchanging the operators and variables in a function, such as replacing AND operator with OR operator and OR operator with AND operator, replacing 0 with 1 and 1 with 0.

So, it states that:

$$(A+B)' = A' \cdot B'$$

$$(A \cdot B)' = A' + B'$$

Show that:  $\overline{ABC} = \overline{A} + \overline{B} + \overline{C}$

• We use truth table:

A	B	C	ABC	$\overline{ABC}$	$\overline{A}$	$\overline{B}$	$\overline{C}$	$\overline{A} + \overline{B} + \overline{C}$
0	0	0	0	1	1	1	1	1
0	0	1	0	1	1	1	0	1
0	1	0	0	1	1	0	1	1
0	1	1	0	1	1	0	0	1
1	0	0	0	1	0	1	1	1
1	0	1	0	1	0	1	0	1
1	1	0	0	1	0	0	1	1
1	1	1	1	0	0	0	0	0

So, from the above table:

Column of  $(\overline{ABC}) = \text{column of } (\overline{A} + \overline{B} + \overline{C})$

Hence,  $\overline{ABC} = \overline{A} + \overline{B} + \overline{C}$

Now, show that :  $((A+B+C)D) = \overline{A}\overline{B}\overline{C} + \overline{D}$

A	B	C	D	(A+B+C)	((A+B+C)D)	$\overline{((A+B+C)D)}$	$\overline{A}\overline{B}\overline{C}$	$\overline{A}\overline{B}\overline{C} + \overline{D}$
0	0	0	0	0	0	1	1	1
0	0	0	1	0	0	1	1	1
0	0	1	0	1	0	1	0	1
0	0	1	1	1	1	0	0	0
0	1	0	0	1	0	1	0	1
0	1	0	1	1	1	0	0	0
0	1	1	0	1	0	1	0	1
0	1	1	1	1	1	0	0	0
1	0	0	0	1	0	1	0	1
1	0	0	1	1	1	0	0	0
1	0	1	0	1	0	1	0	1
1	0	1	1	1	1	0	0	0
1	1	0	0	1	0	1	0	1
1	1	0	1	1	1	0	0	0
1	1	1	0	1	0	1	0	1
1	1	1	1	1	1	0	0	0

So, from the above table we can easily see that

column of  $\overline{((A+B+C)D)}$  = column of  $(\overline{A}\overline{B}\overline{C} + \overline{D})$

Hence,

$$\overline{((A+B+C)D)} = \overline{A}\overline{B}\overline{C} + \overline{D}$$



Ans 3. b)  $F(A, B, C, D) = \sum(0, 1, 2, 3, 6, 7, 9, 13) + \sum_d(11, 15)$

From the above function, we have given the minterms as well as don't care term

$$\sum_m = (0, 1, 2, 3, 6, 7, 9, 13)$$

$$\sum_d = (11, 15)$$

Using the above terms, we construct a kmap

AB \ CD	00	01	11	10
00	1	0	4	12
01	1	1	5	13
11	1	3	7	15
10	1	2	6	14

From the above K-map we can easily see that by using the minterms and don't care terms we form 3 quads.

First quad using  $= \sum(0, 1, 2, 3)$

Second quad using  $= \sum(2, 3, 6, 7)$

Third quad using  $= \sum(13, 9) + \sum_d(11, 15)$

Now, from first quad we get,

$$\overline{A}\overline{B}$$

From second quad we get,

$$\overline{A}C$$

From third quad we get,

$$AD$$


Now we OR ed these terms so that we get the minimized expression



$$Y = \bar{A}\bar{B} + \bar{A}C + AD$$

Here, Y is the output.

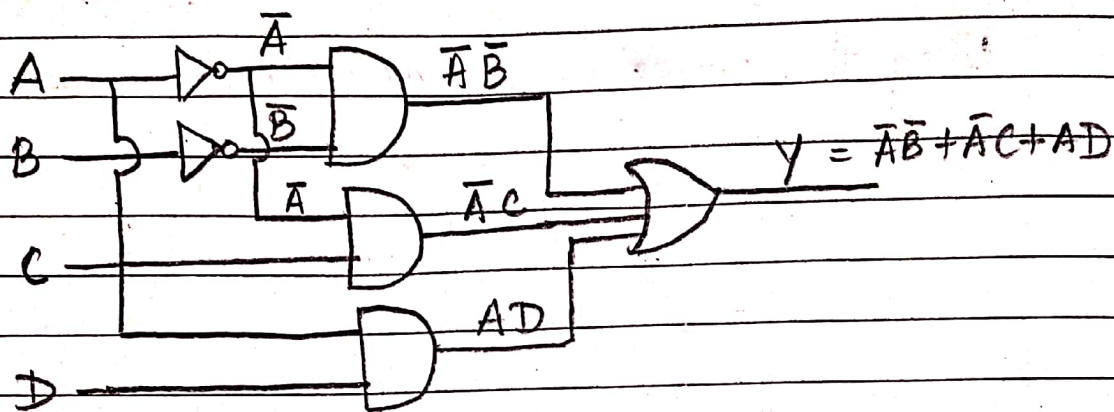Now using this simplified expression we design a circuit.



Here we are using 2 NOT gate, 3-AND Gate and One 3-input OR gate.